

COMP110: Principles of Computing

4: Logic and memory

Learning outcomes

- ▶ **Distinguish** the basic types of logic gate
- ▶ **Use** logic gates to build simple circuits
- ▶ **Explain** how computer memory works

Logic gates


Boolean logic

- ▶ Works with two values: TRUE and FALSE
- ▶ Foundation of the **digital computer**: represented in circuits as **on** and **off**
- ▶ Representing as 1 and 0 leads to **binary notation**
- ▶ One boolean value = one **bit** of information
- ▶ Programmers use boolean logic for conditions in **if** and **while** statements

Not

NOT A is TRUE
if and only if
 A is FALSE


A	NOT A
FALSE	TRUE
TRUE	FALSE

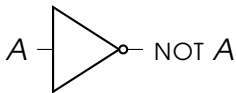

And

A AND B is TRUE
if and only if
both A **and** B are TRUE

A	B	A AND B
FALSE	FALSE	FALSE
FALSE	TRUE	FALSE
TRUE	FALSE	FALSE
TRUE	TRUE	TRUE

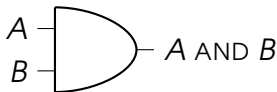

Or

A OR B is TRUE
if and only if
either A **or** B , **or both**, are TRUE

A	B	A AND B
FALSE	FALSE	FALSE
FALSE	TRUE	TRUE
TRUE	FALSE	TRUE
TRUE	TRUE	TRUE



Socratic FALCOMPED

What is the value of

$A \text{ AND } (B \text{ OR } C)$

when

$A = \text{TRUE}$

$B = \text{FALSE}$

$C = \text{TRUE}$

?

Socratic FALCOMPED

What is the value of

$(\text{NOT } A) \text{ AND } (B \text{ OR } C)$

when

$A = \text{TRUE}$

$B = \text{FALSE}$

$C = \text{TRUE}$

?

Socratic FALCOMPED

For what values of A, B, C, D is

$$A \text{ AND NOT } B \text{ AND NOT } (C \text{ OR } D) = \text{TRUE}$$

?

Socratic FALCOMPED

What is the value of

$A \text{ OR NOT } A$

?

Socratic FALCOMPED

What is the value of

$A \text{ AND NOT } A$

?

Socratic FALCOMPED

What is the value of

$A \text{ OR } A$

?

Socratic FALCOMPED


What is the value of

$A \text{ AND } A$

?

Socratic FALCOMPED

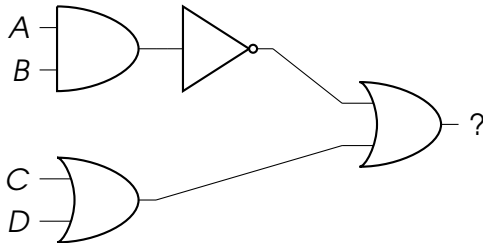What expression is equivalent to this circuit?



Writing logical operations


Operation	Python	C family	Mathematics
NOT A	not a	$!a$	$\neg A$ or \bar{A}
A AND B	a and b	$a \ \&\& \ b$	$A \wedge B$
A OR B	a or b	$a \ \ b$	$A \vee B$

Other operators can be expressed by combining these

Exclusive Or

$A \text{ XOR } B$ is TRUE
if and only if
either A **or** B , **but not both**, are TRUE

A	B	$A \text{ AND } B$
FALSE	FALSE	FALSE
FALSE	TRUE	TRUE
TRUE	FALSE	TRUE
TRUE	TRUE	FALSE

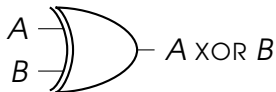

Socratic FALCOMPED

How can $A \text{ XOR } B$ be written using the operations
AND , OR , NOT ?

Negative gates

NAND , NOR , XNOR
are the **negations** of
AND , OR , XOR

$$A \text{ NAND } B = \text{NOT } (A \text{ AND } B)$$

$$A \text{ NOR } B = \text{NOT } (A \text{ OR } B)$$

$$A \text{ XNOR } B = \text{NOT } (A \text{ XOR } B)$$

