



FALMOUTH
UNIVERSITY

GAM160-COMP140 Creative Computing Project

Register Attendance



Figure 1: Attendance monitoring is in place. It is your responsibility to ensure that you have signed yourself in.


Learning Outcomes

After this session you will be able to:

- ▶ **Explain** the difference between current, voltage, and resistance
- ▶ **Predict** the characteristics of basic circuits using simple formulas
- ▶ **Choose** components based on their purpose and characteristics

What is current electricity?


(the stuff that makes our gadgets tick)

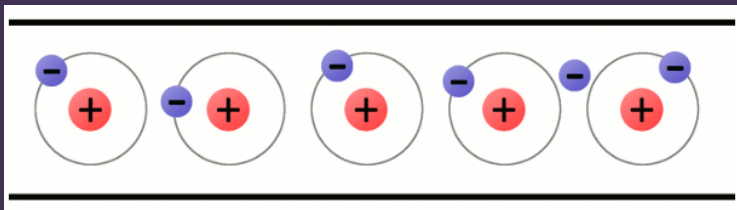

source: <https://learn.sparkfun.com/tutorials/what-is-electricity/allmar>

- ▶ The flow of electrons through
- ▶ a closed circuit (wire, components, etc)
- ▶ Induced by an electric field (battery)

Battery Example

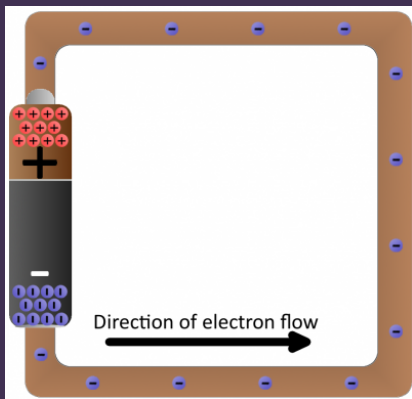

source: <https://learn.sparkfun.com/tutorials/what-is-electricity/allrmar>

Basic characteristics

- ▶ **Voltage (V)** - The relative level of electrical energy between any two points in a circuit. Voltage is measured in *volts*.
- ▶ **Current (I)** - The amount of electrical energy passing through any point in a circuit. Current is measured in *amps*
- ▶ **Resistance (R)** - The amount that any component in the circuit resists the flow of current. Resistance is measured in *ohms*

Water Analogy

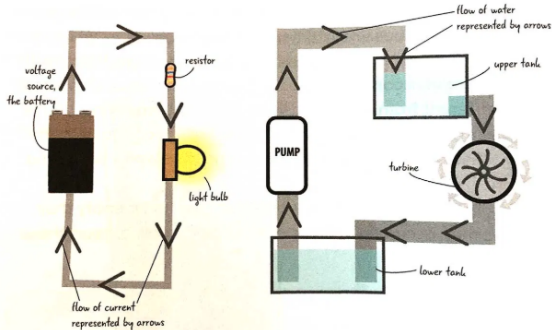


FIGURE 5.34: Water analogy for electricity

Hagan, J. (2017). Learn Electronics with Arduino. Maker Media, Inc.

Ohms Law

$$I = V / R$$