



FALMOUTH
UNIVERSITY



COMP110: Principles of Computing

4: Logic and memory

Worksheet 4

Due **next Friday!**

Logic gates



Boolean logic

- ▶ Works with two values: TRUE and FALSE
- ▶ Foundation of the **digital computer**: represented in circuits as **on** and **off**
- ▶ Representing as 1 and 0 leads to **binary notation**
- ▶ One boolean value = one **bit** of information
- ▶ Programmers use boolean logic for conditions in **if** and **while** statements

Not

NOT A is TRUE
if and only if
 A is FALSE

A	NOT A
FALSE	TRUE
TRUE	FALSE



And

A AND B is TRUE
if and only if
both A **and** B are TRUE

A	B	A AND B
FALSE	FALSE	FALSE
FALSE	TRUE	FALSE
TRUE	FALSE	FALSE
TRUE	TRUE	TRUE



Or

A OR B is TRUE
if and only if
either A **or** B , **or both**, are TRUE

A	B	A AND B
FALSE	FALSE	FALSE
FALSE	TRUE	TRUE
TRUE	FALSE	TRUE
TRUE	TRUE	TRUE



Socratic FALCOMPED

What is the value of

$A \text{ AND } (B \text{ OR } C)$

when

$A = \text{TRUE}$

$B = \text{FALSE}$

$C = \text{TRUE}$

?

Socratic FALCOMPED

What is the value of

$(\text{NOT } A) \text{ AND } (B \text{ OR } C)$

when

$A = \text{TRUE}$

$B = \text{FALSE}$

$C = \text{TRUE}$

?

Socratic FALCOMPED

For what values of A, B, C, D is

$$A \text{ AND NOT } B \text{ AND NOT } (C \text{ OR } D) = \text{TRUE}$$

?

Socratic FALCOMPED

What is the value of

A OR NOT A

?

Socratic FALCOMPED

What is the value of

$A \text{ AND NOT } A$

?

Socratic FALCOMPED

What is the value of

$A \text{ OR } A$

?

Socratic FALCOMPED


What is the value of

$A \text{ AND } A$

?

Socratic FALCOMPED

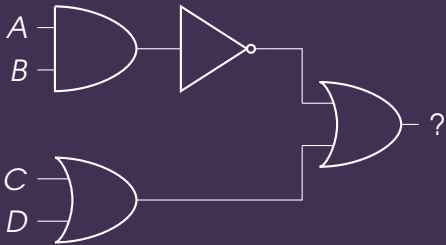What expression is equivalent to this circuit?



Writing logical operations

Operation	Python	C family	Mathematics
NOT A	<code>not</code> a	<code>!a</code>	$\neg A$ or \bar{A}
A AND B	a <code>and</code> b	$a \ \&\& \ b$	$A \wedge B$
A OR B	a <code>or</code> b	$a \ \ b$	$A \vee B$

Other operators can be expressed by combining these

Exclusive Or

$A \text{ XOR } B$ is TRUE
if and only if
either A **or** B , **but not both**, are TRUE

A	B	$A \text{ AND } B$
FALSE	FALSE	FALSE
FALSE	TRUE	TRUE
TRUE	FALSE	TRUE
TRUE	TRUE	FALSE



Socratic FALCOMPED

How can $A \text{ XOR } B$ be written using the operations
AND , OR , NOT ?

BOOLEAN HAIR LOGIC

A



B



AND



OR



XOR


Negative gates

NAND , NOR , XNOR
are the **negations** of
AND , OR , XOR


$$A \text{ NAND } B = \text{NOT } (A \text{ AND } B)$$

$$A \text{ NOR } B = \text{NOT } (A \text{ OR } B)$$

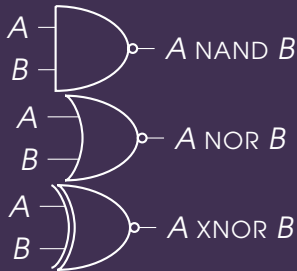
$$A \text{ XNOR } B = \text{NOT } (A \text{ XOR } B)$$



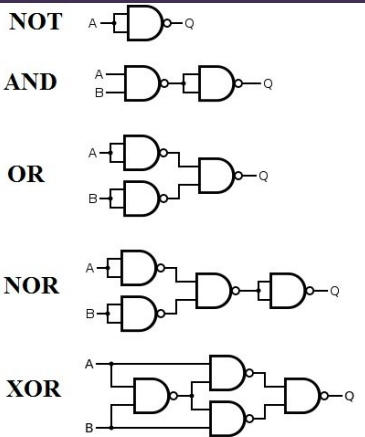Any logic gate can be constructed from NAND gates



What does this circuit do?

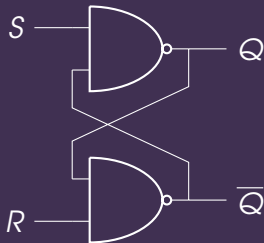

- ▶ This is called a **NAND latch**
- ▶ It “remembers” a single boolean value
- ▶ Put a few billion of these together (along with some control circuitry) and you’ve got **memory**!


NAND gates

- ▶ All arithmetic and logic operations, as well as memory, can be built from NAND gates
- ▶ So an entire computer can be built just from NAND gates!
- ▶ Play the game: <http://nandgame.com>
- ▶ NAND gate circuits are **Turing complete**
- ▶ The same is true of NOR gates

Arithmetic Logic Unit



Arithmetic Logic Unit

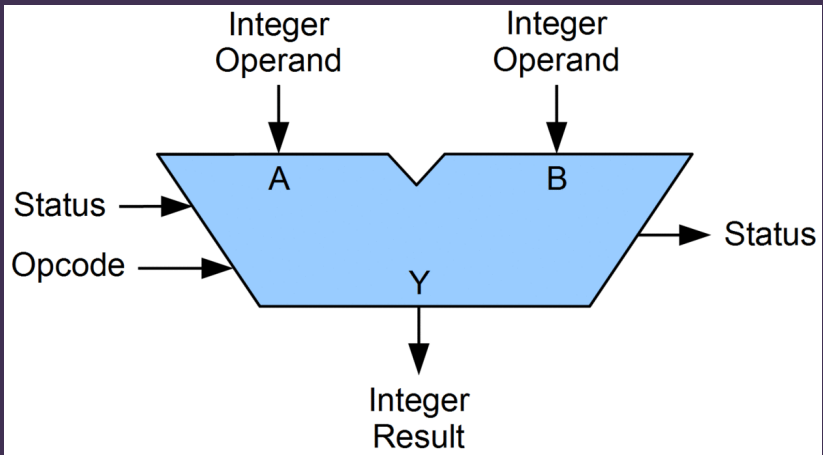

Arithmetic Logic Unit

- ▶ Important part of the CPU
- ▶ Inputs:
 - ▶ **Operand** words A, B
 - ▶ **Opcode**
 - ▶ **Status** bits
- ▶ Outputs:
 - ▶ **Result** word Y
 - ▶ **Status** bits
- ▶ Opcode specifies how Y is calculated based on A and B

ALU operations


Typically include:

- ▶ Add with carry
- ▶ Subtract with borrow
- ▶ Negate (2's complement)
- ▶ Increment, decrement
- ▶ Bitwise AND, OR, NOT, ...
- ▶ Bit shifts

Adding 3 bits

A	B	C	$A + B + C$
0	0	0	00
0	0	1	01
0	1	0	01
0	1	1	10
1	0	0	01
1	0	1	10
1	1	0	10
1	1	1	11

1-bit adder

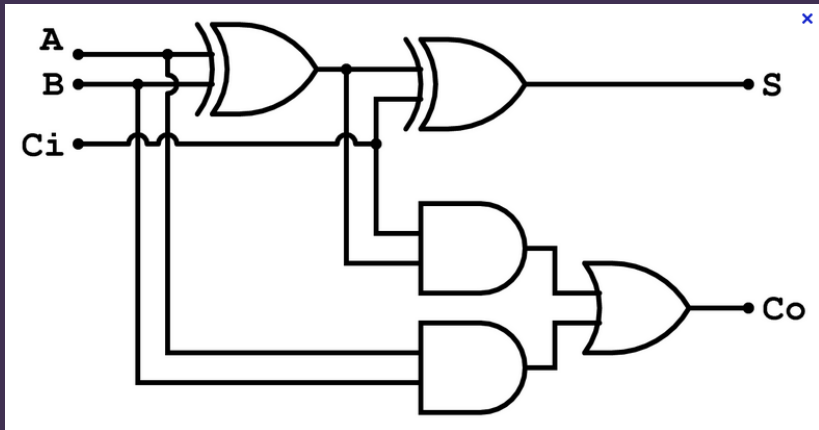

How does the 1-bit adder work?

Exercise:

- ▶ Write down the boolean expressions for S and C_o
- ▶ Draw a truth table for these
- ▶ Compare the truth table to the addition table on a previous slide

n -bit adder

