



COMP110: Principles of Computing

4: Session title here

Learning outcomes

- ▶ **Distinguish** the basic types of logic gate
- ▶ **Use** logic gates to build simple circuits
- ▶ **Explain** how computer memory works

Logic gates



Boolean logic

- ▶ Works with two values: TRUE and FALSE

Not

A	NOT A
FALSE	TRUE
TRUE	FALSE

NOT A is TRUE
if and only if
A is FALSE

And

A	B	$A \text{ AND } B$
FALSE	FALSE	FALSE
FALSE	TRUE	FALSE
TRUE	FALSE	FALSE
TRUE	TRUE	TRUE

$A \text{ AND } B$ is TRUE
if and only if
both A **and** B are TRUE

Or

A	B	$A \text{ OR } B$
FALSE	FALSE	FALSE
FALSE	TRUE	TRUE
TRUE	FALSE	TRUE
TRUE	TRUE	TRUE

$A \text{ OR } B$ is TRUE
if and only if
either A or B or both are TRUE

Exclusive-or

A	B	$A \text{ XOR } B$
FALSE	FALSE	FALSE
FALSE	TRUE	TRUE
TRUE	FALSE	TRUE
TRUE	TRUE	FALSE

$A \text{ XOR } B$ is TRUE
if and only if
either A or B , but not both
are TRUE