



FALMOUTH  
UNIVERSITY



# COMP110: Principles of Computing

## 4: Logic and memory

# Learning outcomes

- ▶ **Distinguish** the basic types of logic gate
- ▶ **Use** logic gates to build simple circuits
- ▶ **Explain** how computer memory works

# Logic gates



# Boolean logic

- ▶ Works with two values: TRUE and FALSE
- ▶ Foundation of the **digital computer**: represented in circuits as **on** and **off**
- ▶ Representing as 1 and 0 leads to **binary notation**
- ▶ One boolean value = one **bit** of information
- ▶ Programmers use boolean logic for conditions in **if** and **while** statements

# Not

NOT  $A$  is TRUE  
if and only if  
 $A$  is FALSE

$A$	NOT $A$
FALSE	TRUE
TRUE	FALSE



# And

$A$  AND  $B$  is TRUE  
if and only if  
**both**  $A$  **and**  $B$  are TRUE

$A$	$B$	$A$ AND $B$
FALSE	FALSE	FALSE
FALSE	TRUE	FALSE
TRUE	FALSE	FALSE
TRUE	TRUE	TRUE



# Or

$A$  OR  $B$  is TRUE  
if and only if  
**either**  $A$  **or**  $B$ , **or both**, are TRUE

$A$	$B$	$A$ AND $B$
FALSE	FALSE	FALSE
FALSE	TRUE	TRUE
TRUE	FALSE	TRUE
TRUE	TRUE	TRUE



# Socratic FALCOMPED

What is the value of

$A \text{ AND } (B \text{ OR } C)$

when

$A = \text{TRUE}$

$B = \text{FALSE}$

$C = \text{TRUE}$

?



# Socratic FALCOMPED

What is the value of

$(\text{NOT } A) \text{ AND } (B \text{ OR } C)$

when

$A = \text{TRUE}$

$B = \text{FALSE}$

$C = \text{TRUE}$

?

# Socratic FALCOMPED

For what values of  $A, B, C, D$  is

$$A \text{ AND NOT } B \text{ AND NOT } (C \text{ OR } D) = \text{TRUE}$$

?

# Socratic FALCOMPED

What is the value of

A OR NOT A

?

# Socratic FALCOMPED

What is the value of

$A \text{ AND NOT } A$

?

# Socratic FALCOMPED

What is the value of

$A \text{ OR } A$

?

# Socratic FALCOMPED


What is the value of

$A \text{ AND } A$

?
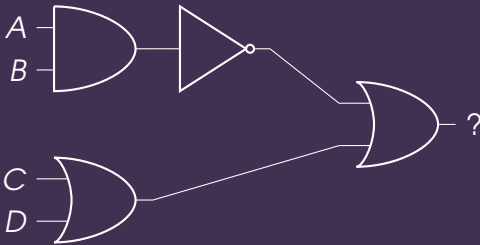
# Socratic FALCOMPED

What expression is equivalent to this circuit?



# Writing logical operations

Operation	Python	C family	Mathematics
NOT $A$	<code>not</code> $a$	<code>!a</code>	$\neg A$ or $\bar{A}$
$A$ AND $B$	$a$ <code>and</code> $b$	$a \ \&\& \ b$	$A \wedge B$
$A$ OR $B$	$a$ <code>or</code> $b$	$a \    \ b$	$A \vee B$

Other operators can be expressed by combining these



# Exclusive Or

$A \text{ XOR } B$  is TRUE  
if and only if  
**either**  $A$  **or**  $B$ , **but not both**, are TRUE

$A$	$B$	$A \text{ AND } B$
FALSE	FALSE	FALSE
FALSE	TRUE	TRUE
TRUE	FALSE	TRUE
TRUE	TRUE	FALSE



# Socratic FALCOMPED

How can  $A \text{ XOR } B$  be written using the operations  
AND , OR , NOT ?


# Negative gates

NAND , NOR , XNOR  
are the **negations** of  
AND , OR , XOR


$$A \text{ NAND } B = \text{NOT } (A \text{ AND } B)$$

$$A \text{ NOR } B = \text{NOT } (A \text{ OR } B)$$

 
$$A \text{ XNOR } B = \text{NOT } (A \text{ XOR } B)$$


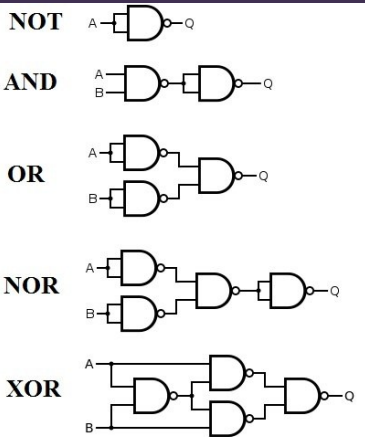
# Any logic gate can be constructed from NAND gates



# What does this circuit do?

 

- ▶ This is called a **NAND latch**
- ▶ It “remembers” a single boolean value
- ▶ Put a few billion of these together (along with some control circuitry) and you’ve got **memory**!


# NAND gates

- ▶ All arithmetic and logic operations, as well as memory, can be built from NAND gates
- ▶ So an entire computer can be built just from NAND gates!
- ▶ Play the game: <http://nandgame.com>
- ▶ NAND gate circuits are **Turing complete**
- ▶ The same is true of NOR gates

# Arithmetic Logic Unit



# Arithmetic Logic Unit

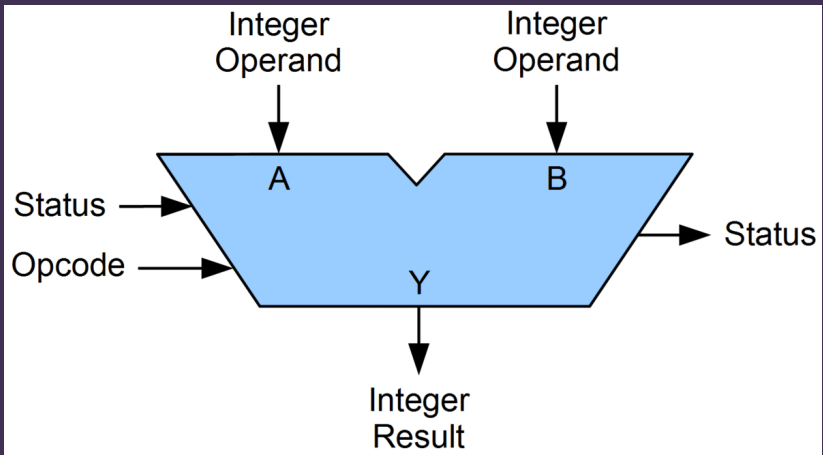



# Arithmetic Logic Unit

- ▶ Important part of the CPU
- ▶ Inputs:
  - ▶ **Operand** words  $A, B$
  - ▶ **Opcode**
  - ▶ **Status** bits
- ▶ Outputs:
  - ▶ **Result** word  $Y$
  - ▶ **Status** bits
- ▶ Opcode specifies how  $Y$  is calculated based on  $A$  and  $B$

# ALU operations


Typically include:

- ▶ Add with carry
- ▶ Subtract with borrow
- ▶ Negate (2's complement)
- ▶ Increment, decrement
- ▶ Bitwise AND, OR, NOT, ...
- ▶ Bit shifts

# Adding 3 bits

$A$	$B$	$C$	$A + B + C$
0	0	0	00
0	0	1	01
0	1	0	01
0	1	1	10
1	0	0	01
1	0	1	10
1	1	0	10
1	1	1	11

# 1-bit adder

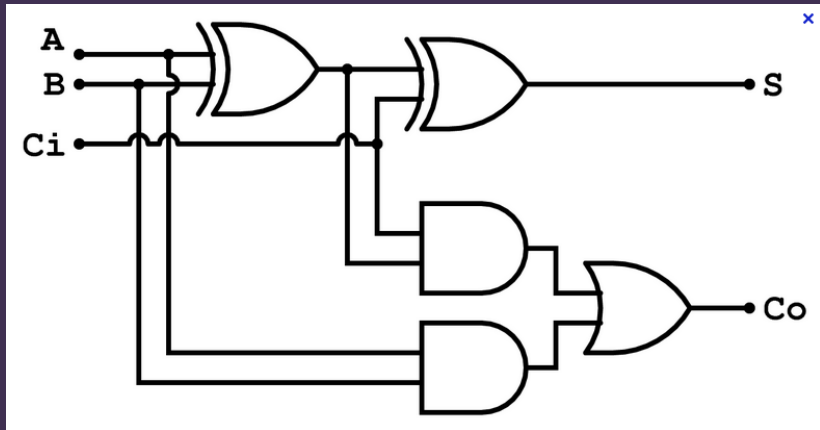


# How does the 1-bit adder work?

Exercise:

- ▶ Write down the boolean expressions for  $S$  and  $C_o$
- ▶ Draw a truth table for these
- ▶ Compare the truth table to the addition table on a previous slide

# $n$ -bit adder

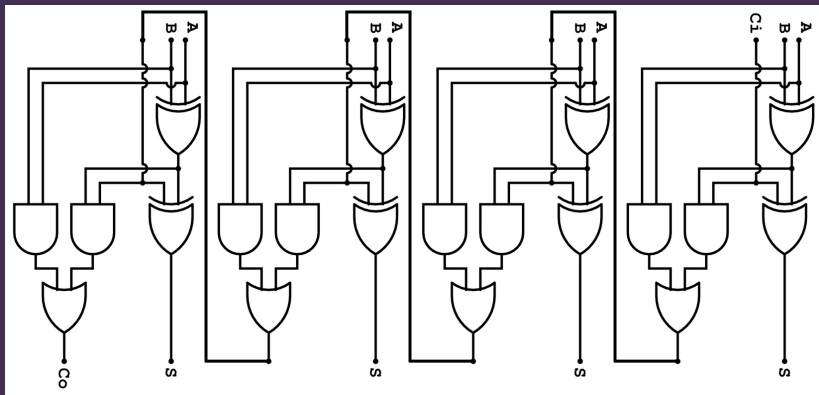

# Exercise Sheet ii

Due **next Tuesday!**